

34 Current electricity

A34.1

What is an electric current?

The flow of electrons through a wire


A34.2

- (a) Draw a circuit diagram you could use to identify if a substance is a conductor of electricity.
 (b) How would you know if a substance is a good conductor of electricity or a poor conductor?

If the light goes on

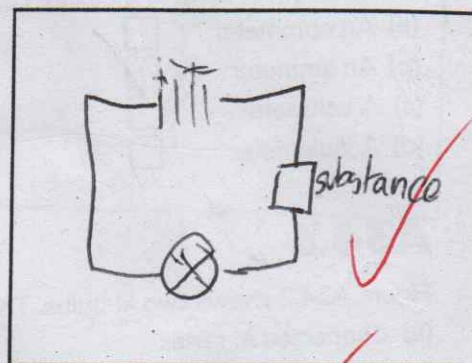- (c) Underline which of the following conduct electricity:

euro coin plastic pen metal paperclip
brass key graphite in a pencil water



- (d) What term is given to a substance that does not conduct electricity?

insulator

- (e) Give a use for such a substance.

protection on electrical wiring


- (f) Name the circuit symbols shown in Table A34.1.

Symbol	Name
	<u>Light emitting diode</u>
	<u>Resistor</u>
	<u>Switch</u>
	<u>Ohmmeter</u>
	<u>Battery</u>

Table A34.1

A34.3

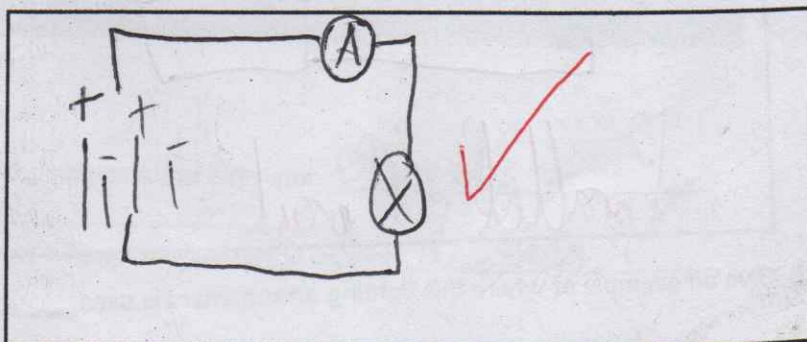In the box provided draw a circuit diagram of a bulb in a circuit with a battery and an appropriate instrument used to measure the current flowing in the circuit.



A34.4

The circuit symbol in Figure A34.1 is the symbol for:

- (a) A fixed resistor ☐
 (b) A bulb ☐
 (c) A light-emitting diode ☒
 (d) An ohmmeter ☐



Figure A34.1

A34.5

The instrument used to measure current is called:

- (a) An ohmmeter ☐
 (b) An ammeter ☒
 (c) A voltmeter ☐
 (d) A joulemeter ☐

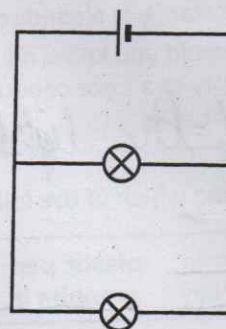


Figure A34.2

A34.6

Figure A34.2 shows two lit bulbs. The bulbs are:

- (a) Connected in series ☐
 (b) Connected in parallel ☒
 (c) Connected one in series and one in parallel ☐
 (d) Not connected ☐

A34.7

- (a) What term is used to describe the arrangement of bulbs in Figure A34.3?

Series

- (b) If one bulb blows, the other bulb stops lighting. Explain why this is the case.

Because current can no longer pass through the blown bulb


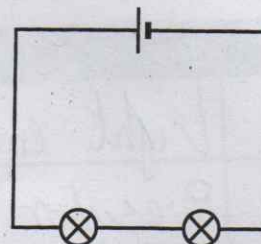


Figure A34.3

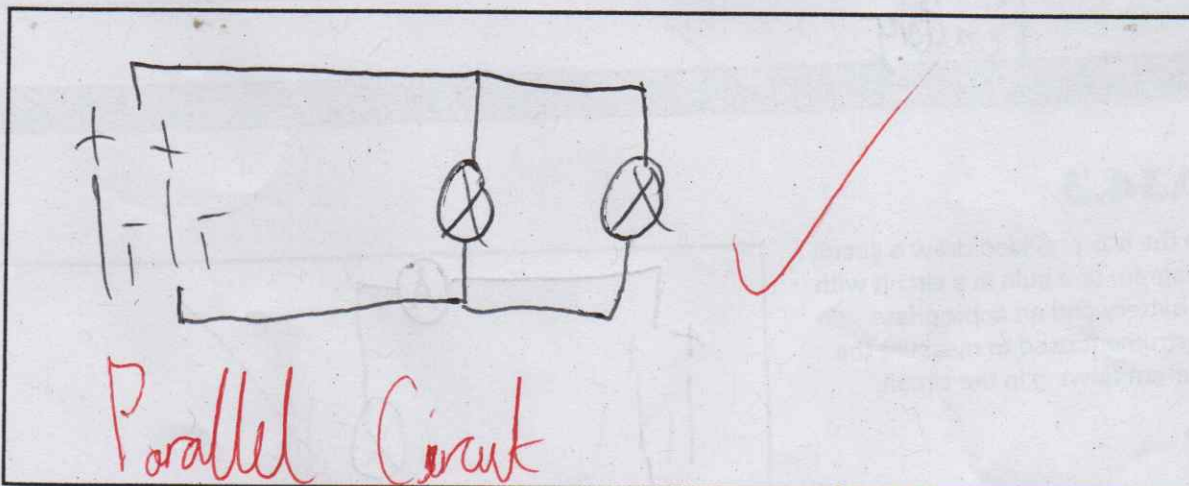- (c) Draw an alternative arrangement of the circuit so that if one bulb blows the other will remain lighting.




- (d) Give an example of where this lighting arrangement is used.

Car lights
I didn't see this question


A34.8

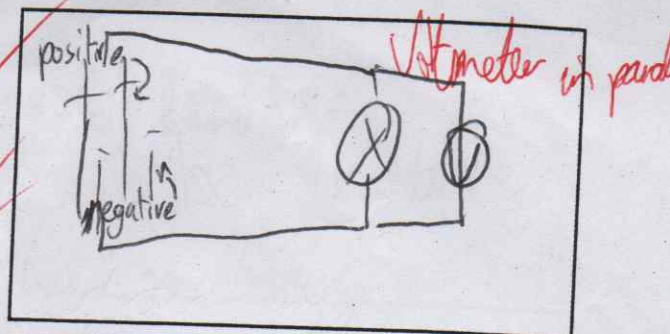- (a) In the box provided draw a circuit diagram of a bulb and a battery so the bulb lights up. ✓
 (b) Draw a voltmeter connected correctly to measure the potential difference across the bulb. ✓
 (c) In the diagram indicate the positive side and negative side of the battery symbol. ✓



A34.9

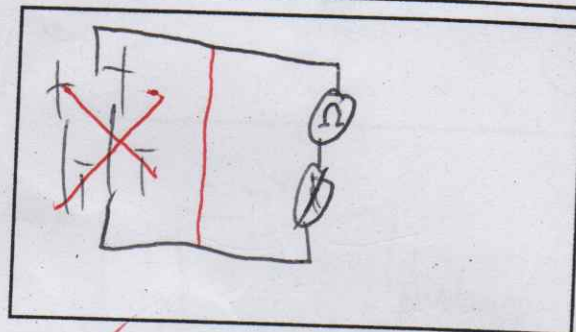- (a) Draw a circuit diagram of the apparatus used to measure the resistance of a light bulb. ✓
 (b) What are the units of resistance? ohm ✓



A34.10


In Figure A34.4, the circuit symbol for a battery is:

(a) Symbol 1 ☐

(b) Symbol 2 ☒

(c) Symbol 3 ☐

(d) Symbol 4 ☐

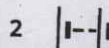

A34.11

The device used for measuring potential difference = voltage is known as:

(a) A variable resistor ☐

(b) An ammeter ☐

(c) A voltmeter ☒

(d) An ohmmeter ☐

Figure A34.4

A34.12

Name the instruments represented by the symbols shown in Table A34.2.

Symbol	Name
	<u>Resistor Fixed resistor</u>
	<u>Variable resistor</u>
	<u>Light dependent resistor</u> <u>Street lamps</u>
	<u>Thermistor</u> <u>Heat</u>

Table A34.2

A34.13

- (a) Name the instrument used to measure the resistance of a resistor. Ohmmeter ✓
 (b) What is the unit of resistance? ohm ✓
 (c) For a constant voltage, if the resistance of a circuit increases, the current decreases ✓